




## 2.4 Electric Circuits

This topic covers the definitions of various electrical quantities, for example current, potential difference and resistance, Ohm's law and non-ohmic conductors, potential dividers, e.m.f. and internal resistance of cells and negative temperature coefficient thermistors.

This topic should be studied using applications such as space technology.

This unit includes many opportunities for developing experimental skills and techniques by carrying out more than just the core practical experiments.

**Candidates will be assessed on their ability to:**
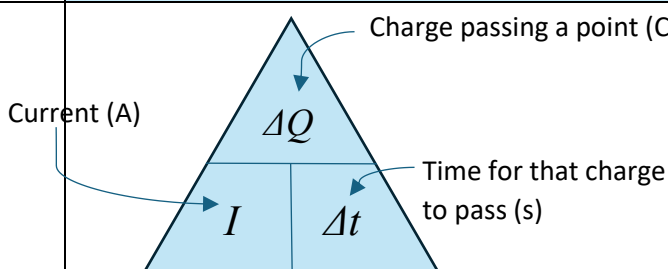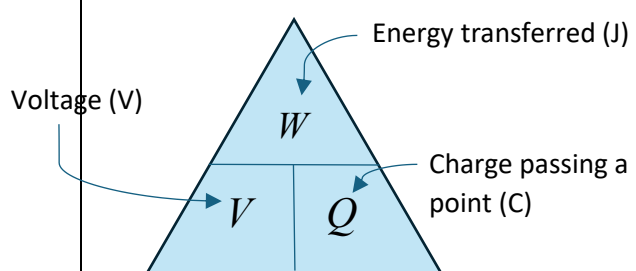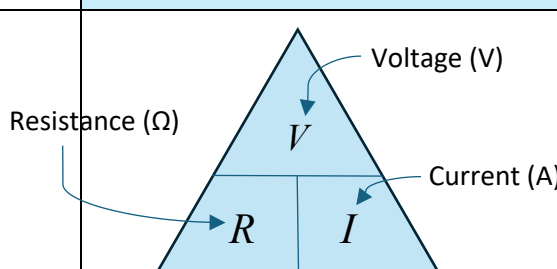
<b>64</b>	understand that electric current is the rate of flow of charged particles and be able to use the equation $I = \frac{\Delta Q}{\Delta t}$
Current (A)	 <div> <p><b>Electric current</b> is the rate of flow of charged particles</p> </div>
<b>65</b>	understand how to use the equation $V = \frac{W}{Q}$
Voltage (V)	 <div> <p><b>Voltage</b> is the energy transferred per unit charge</p> </div>
<b>66</b>	understand that resistance is defined by $R = \frac{V}{I}$ and that Ohm's law is a special case when $I \propto V$ for constant temperature
Resistance (Ω)	 <div> <p><b>Resistance</b> is the opposition to the flow of current</p> <p>Ohm's law states that the current through a component is directly proportional to the voltage across it, provided that the temperature remains constant <b><math>V = IR</math></b></p> </div>

67	(a) understand how the distribution of current in a circuit is a consequence of charge conservation (b) understand how the distribution of potential differences in a circuit is a consequence of energy conservation																
(a)	The total amount of charge within a circuit cannot increase or decrease while the circuit is functioning due to conservation of charge At a junction, current will split (current is more likely to take the path with the lesser resistance) and when they join up again, Sum of current entering a junction = Sum of current leaving a junction																
(b)	In a closed-circuit loop (series circuit), Total sum of emfs = Total sum of potential difference around that loop Due to the law of conservation of energy, energy is never used up or lost in a circuit																
68	be able to derive the equations for combining resistances in series and parallel using the principles of charge and energy conservation, and be able to use these equations																
	<table><tr><th>Formula Derivation for <math>R_{\text{total}}</math> in Series</th><th>Formula Derivation for <math>R_{\text{total}}</math> in Parallel</th></tr><tr><td>In series circuit, <math>V_{\text{total}} = V_1 + V_2</math> Current is the same throughout <math>\Rightarrow IR_{\text{total}} = IR_1 + IR_2</math> <math>IR_{\text{total}} = I(R_1 + R_2)</math> <math>R_{\text{total}} = R_1 + R_2</math></td><td>In parallel circuit, <math>I_{\text{total}} = I_1 + I_2</math> <math>\frac{V}{R_{\text{total}}} = \frac{V_1}{R_1} + \frac{V_2}{R_2}</math> Voltage is same in parallel so <math>\div V \Rightarrow \frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2}</math></td></tr></table> <table><tr><th>Quantity</th><th>Series Circuit Rules</th><th>Parallel Circuit Rules</th></tr><tr><td>Current</td><td>Current is the same throughout</td><td><math>I_{\text{total}} = I_1 + I_2</math></td></tr><tr><td>Voltage</td><td><math>V_{\text{total}} = V_1 + V_2</math></td><td>Voltage is the same on each branch</td></tr><tr><td>Resistance</td><td><math>R_{\text{total}} = R_1 + R_2</math></td><td><math>\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2}</math></td></tr></table>	Formula Derivation for $R_{\text{total}}$ in Series	Formula Derivation for $R_{\text{total}}$ in Parallel	In series circuit, $V_{\text{total}} = V_1 + V_2$ Current is the same throughout $\Rightarrow IR_{\text{total}} = IR_1 + IR_2$ $IR_{\text{total}} = I(R_1 + R_2)$ $R_{\text{total}} = R_1 + R_2$	In parallel circuit, $I_{\text{total}} = I_1 + I_2$ $\frac{V}{R_{\text{total}}} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$ Voltage is same in parallel so $\div V \Rightarrow \frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2}$	Quantity	Series Circuit Rules	Parallel Circuit Rules	Current	Current is the same throughout	$I_{\text{total}} = I_1 + I_2$	Voltage	$V_{\text{total}} = V_1 + V_2$	Voltage is the same on each branch	Resistance	$R_{\text{total}} = R_1 + R_2$	$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2}$
Formula Derivation for $R_{\text{total}}$ in Series	Formula Derivation for $R_{\text{total}}$ in Parallel																
In series circuit, $V_{\text{total}} = V_1 + V_2$ Current is the same throughout $\Rightarrow IR_{\text{total}} = IR_1 + IR_2$ $IR_{\text{total}} = I(R_1 + R_2)$ $R_{\text{total}} = R_1 + R_2$	In parallel circuit, $I_{\text{total}} = I_1 + I_2$ $\frac{V}{R_{\text{total}}} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$ Voltage is same in parallel so $\div V \Rightarrow \frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2}$																
Quantity	Series Circuit Rules	Parallel Circuit Rules															
Current	Current is the same throughout	$I_{\text{total}} = I_1 + I_2$															
Voltage	$V_{\text{total}} = V_1 + V_2$	Voltage is the same on each branch															
Resistance	$R_{\text{total}} = R_1 + R_2$	$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2}$															
69	be able to use the equations $P = VI$ , $W = VIt$ and be able to derive and use related equations, e.g. $P = I^2R$ and $P = \frac{V^2}{R}$																

70	understand how to sketch, recognise and interpret current-potential difference graphs for components, including ohmic conductors, filament bulbs, thermistors and diodes
	<div style="display: flex; flex-wrap: wrap;"> <div style="width: 50%;"> <p style="text-align: center;"><b>FILAMENT LAMP</b></p> <p style="text-align: center;"><small>Copyright © Save My Exams. All Rights Reserved</small></p> </div> <div style="width: 50%;"> <p style="text-align: center;"><b>RESISTOR</b></p> <p style="text-align: center;"><small>Copyright © Save My Exams. All Rights Reserved</small></p> </div> <div style="width: 50%;"> <p style="text-align: center;"><b>SEMICONDUCTOR DIODE</b></p> <p style="text-align: center;"><small>All Rights Reserved</small></p> </div> <div style="width: 50%;"> <p style="text-align: center;"><b>THERMISTOR</b></p> <p style="text-align: center;"><small>Copyright © Save My Exams. All Rights Reserved</small></p> </div> </div>
71	be able to use the equation $R = \frac{\rho l}{A}$
	<p style="text-align: center;"><small>Copyright © Save My Exams. All Rights Reserved</small></p>
72	<b>CORE PRACTICAL 7: Determine the electrical resistivity of a material</b>
73	be able to use $I = nqvA$ to explain the large range of resistivities of different materials
74	understand how the potential along a uniform current-carrying wire varies with the distance along it
	<p>At a constant temperature, as the length of a uniform conductor increases, resistance also increases          As <math>V=IR</math>, as <math>R</math> increases, <math>V</math> also increases          Hence, potential difference across a uniform wire is directly proportional to its length</p>

<p><b>75</b></p>	<p>understand the principles of a potential divider circuit and understand how to calculate potential differences and resistances in such a circuit</p> <div data-bbox="295 235 861 302" style="border: 1px solid black; padding: 5px;"> <p>POTENTIAL DIVIDER EQUATION: <math>V_{out} = \frac{R_2}{R_1 + R_2} V_{in}</math></p> </div> <div data-bbox="375 336 829 772"> </div> <div data-bbox="869 246 1476 571"> <div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>LDR POTENTIAL DIVIDER CIRCUIT</p> </div> <div style="text-align: center;"> <p>THERMISTOR POTENTIAL DIVIDER CIRCUIT</p> </div> </div> </div> <div data-bbox="917 604 1460 750" style="border: 1px solid black; padding: 10px;"> <p>Potential dividers are circuits that divide voltage of the power supply in a certain ratio using two resistors in series</p> </div> <p>If the resistance of one of the resistors is increased, the potential difference across that resistor will increase whilst the potential difference across the other resistor will decrease  We can also link the ratio of p.d. and resistance across each resistor using: <math>\frac{V_1}{V_2} = \frac{R_1}{R_2}</math></p>						
<p><b>76</b></p>	<p>be able to analyse potential divider circuits where one resistance is variable including thermistors and light dependent resistors (LDRs)</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td data-bbox="295 1041 742 1355" style="text-align: center;"> </td><td data-bbox="742 1041 1497 1355"> <p><u>Potentiometer</u></p> <p>If the slider in the diagram is moved upwards, the resistance of the lower part will increase and so the potential difference across it will increase</p> </td></tr> <tr> <td data-bbox="295 1355 742 1657" style="text-align: center;"> </td><td data-bbox="742 1355 1497 1657"> <p><u>Thermistor</u></p> <p>When temperature increases, resistance of thermistor decreases, the potential difference across the thermistor also decreases which means the potential difference across the other resistor increases</p> </td></tr> <tr> <td data-bbox="295 1657 742 1960" style="text-align: center;"> </td><td data-bbox="742 1657 1497 1960"> <p><u>Light Intensity</u></p> <p>When light intensity increases, resistance of LDR decreases, the potential difference across the LDR also decreases which means the potential difference across the other resistor increases</p> </td></tr> </table>		<p><u>Potentiometer</u></p> <p>If the slider in the diagram is moved upwards, the resistance of the lower part will increase and so the potential difference across it will increase</p>		<p><u>Thermistor</u></p> <p>When temperature increases, resistance of thermistor decreases, the potential difference across the thermistor also decreases which means the potential difference across the other resistor increases</p>		<p><u>Light Intensity</u></p> <p>When light intensity increases, resistance of LDR decreases, the potential difference across the LDR also decreases which means the potential difference across the other resistor increases</p>
	<p><u>Potentiometer</u></p> <p>If the slider in the diagram is moved upwards, the resistance of the lower part will increase and so the potential difference across it will increase</p>						
	<p><u>Thermistor</u></p> <p>When temperature increases, resistance of thermistor decreases, the potential difference across the thermistor also decreases which means the potential difference across the other resistor increases</p>						
	<p><u>Light Intensity</u></p> <p>When light intensity increases, resistance of LDR decreases, the potential difference across the LDR also decreases which means the potential difference across the other resistor increases</p>						

77

**E.m.f.** isn't actually a force but rather a measure of energy transferred per charge (measured in volts)


know the definition of *electromotive force (e.m.f.)* and understand what is meant by *internal resistance* and know how to distinguish between e.m.f. and *terminal potential difference*

**Electromotive force** is defined as:

"The amount of chemical energy converted into electrical energy per unit charge (when charge passes through a power supply)"

In essence, electromotive force is the work done moving a unit charge around the whole circuit

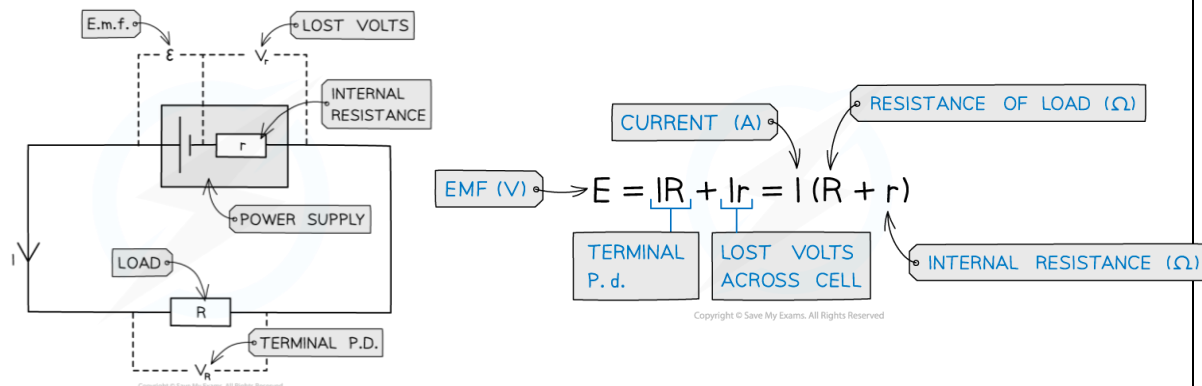Internal resistance is the resistance of an e.m.f. source



78

**CORE PRACTICAL 8: Determine the e.m.f. and internal resistance of an electrical cell**

79

understand how changes of resistance with temperature may be modelled in terms of lattice vibrations and number of conduction electrons and understand how to apply this model to metallic conductors and negative temperature coefficient thermistors

All materials have some resistance to the flow of charge

This is because as free electrons move through a wire, they collide with the metal ions, losing energy as heat

As temperature increases, the vibrations of the ions in the lattice also increase which increases the rate of collisions between free electrons and metal ions. Drift velocity of electrons decreases which results in a decrease in current. As  $V = IR$ , a decrease in current causes an increase in resistance

That is why too high a current will cause an increase in temperature and thus an increase in resistance

**For metallic conductors,**

As temperature increases, resistance (and resistivity) increases and current decreases

As temperature decreases, resistance (and resistivity) decreases and current increases

**For semiconductors (thermistors),**

As temperature increases, the number density of charge carriers (electrons) increases, i.e. the number of conduction electrons per unit volume increases which results in a decrease in resistance (and resistivity)

80

understand how changes of resistance with illumination may be modelled in terms of the number of conduction electrons and understand how to apply this model to LDRs

As the light intensity falling on an LDR increases, more electrons are moved from the valence band to the conduction band which leads to an increase in conduction electrons which in turn results in a decrease in resistance of LDR

# Electrical circuit symbols


Description	Symbol	Description	Symbol
Conductors crossing with no connection		Heater	
Junction of conductors		Thermistor	
Open switch		Light-dependent resistor (LDR)	
Cell		Diode	
Battery of cells		Light-emitting diode (LED)	
Power supply (DC)		Lamp	
Power supply (AC)		Loudspeaker	
Transformer		Microphone	
Ammeter		Electric bell	
Voltmeter		Earth or ground	
Fixed resistor		Motor	
Variable resistor		Generator	
		Fuse/circuit breaker	

Although these are the forms of circuit symbols that will be used in examination papers, there may be other internationally agreed symbols that are acceptable in student answers.
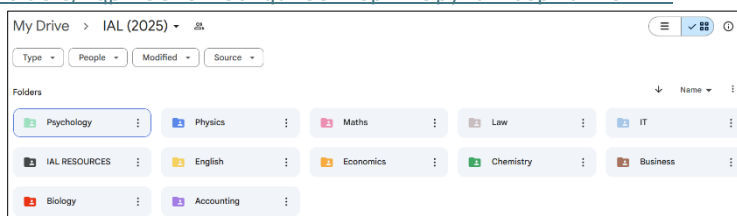
## Remarks

- Disclaimer: This Self-Study Booklet series are NOT intended as a textbook replacement but instead are meant to be used alongside it
- This booklet is primarily exam-based and has been produced to remove unnecessary information from the book to make it into a simpler and more compact form factor
- You are encouraged to regularly check the google drive for updated versions of this booklet (This mean if you have downloaded it at a certain period of time, you should check the drive 3 or 4 months later to see if it has been updated or not)
- Thank you all for using this Self-Study Booklet and if you would like to find more resources like this one, do check out this google drive:  
[https://drive.google.com/drive/folders/1qpY-sGR9iinJbnquB53hx8pLk49pyxd1?usp=drive\\_link](https://drive.google.com/drive/folders/1qpY-sGR9iinJbnquB53hx8pLk49pyxd1?usp=drive_link)
- You will be redirected here:

(Note that there are only Self-Study Booklets/ CAQs for Physics and Chemistry)



- Do keep in mind that this is still a work-in-progress and you are welcome to add more resources to it- just drop a text at @aeth\_en on discord!

## Importance notice regarding Usage Rights

- There are certain images and illustrations used in this document that have been sourced from many different sources. The ownership of these images and/or illustrations belong to their rightful owners
- I do not own these images and/or illustrations
- Reprinting or Copying of this document and Selling/ Profiting will NOT be tolerated
- This Self-Study Booklet is intended for students worldwide studying for the Edexcel International A-Levels and will remain free of charge indefinitely

## Help us improve

- This booklet is in its first edition so it may contain mistakes here and there
- Please let us know of any room for improvement so that we can make it better!
- Contact: [mth.2021education@gmail.com](mailto:mth.2021education@gmail.com) or @aeth\_en on discord
- Best of luck in your A-Levels journey!!